



# Welcome to The Logic Design Lab!

Fall 2021  
Sequential Circuit I

Prof. Chun-Yi Lee

Department of Computer Science  
National Tsing Hua University

# Announcement

- Lab
  - Lab 2 is due on **10/14/2021** (**Thu**)

# Agenda

- **Combinational circuits**
- Sequential circuits
- Debounce circuit and one-pulse circuit
- 7-segment display

## Today's class will help you:

1. Understand the difference between latch and flip-flop
2. Understand the timing diagram of latch and flip-flop
3. Understand synchronous reset
4. Understand the usage of push buttons, debounce circuit, and one-pulse circuit
5. Understand how to display four different digits on a 7-segment display

# Combinational Circuits (1/2)

- You have **three ways** to model a combinational circuit
  - You will be good if you remember them

## 1. Gate-level modeling

- `not N1(out, in);`
- `nand N2(out, in1, in2);`
- `or N3(out, in1, in2, in3);`
- etc.

## 2. Continuous assignment

- Declare your **lvalues** as **wire** data type
- **assign** lvalue = (your logic expression);

# Combinational Circuits (2/2)

## 3. Use always block

- Declare your **lvalues** as **reg** data type
- Only use "=" in your assignment expressions
- Avoid using "<=" in your expressions

### Correct

```
reg lvalue;  
  
always @ (*)  
begin  
    lvalue = (your expression);  
end
```



### Wrong

```
wire lvalue;  
  
always @ (*)  
begin  
    assign lvalue <= (your expression);  
end
```



1. lvalue should be **reg**
2. Can't use **assign**
3. Avoid "<="



# Agenda


- Combinational circuits
  - **Sequential circuits**
  - Debounce circuit and one-pulse circuit
  - 7-segment display
- **Latch and flip-flop**
  - Always block usage
  - Reset

## Today's class will help you:


1. Understand the difference between latch and flip-flop
2. Understand the timing diagram of latch and flip-flop
3. Understand synchronous reset
4. Understand the usage of push buttons, debounce circuit, and one-pulse circuit
5. Understand how to display four different digits on a 7-segment display
 
# Behavioral Modeling

- High level description
- Modeling a circuit by its behaviors
- Similar to C++ programming
- Behavioral modeling includes both **combinational** and **sequential** parts



**Combinational only**

 

**Combinational and Sequential**

# What is Sequential Circuit?


	Sequential	Combinational
Clock	Yes	No
Memory elements	Yes	No
Always block assignment	Non-blocking <=	Blocking =
Continuous assignment	Not available	assign lvalue = rvalue

- Memory element
  - Stores "1" or "0"
  - Latch and Flip-Flop
  - Usually triggered by clock signals




# Basic Sequential Circuit

D Flip-Flop

 

 
```
always @ (posedge clk)
begin
    //Non-blocking assignment
    Out <= In;
end
```




# Latch and D Flip-Flop

- **Latch:** triggered by **level**

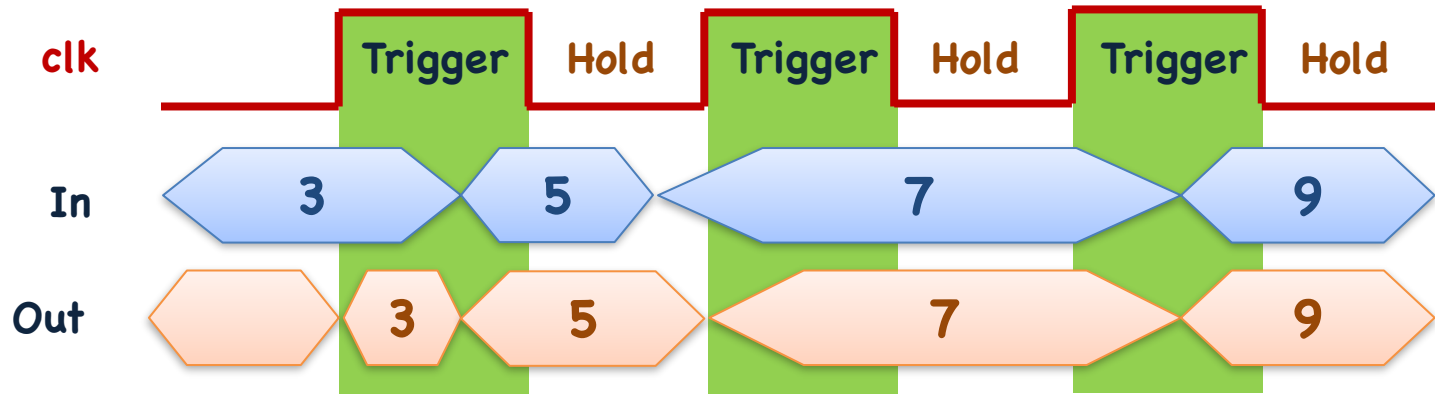

 - **D Flip-Flop:** triggered by **clock edge**



# D Flip Flop

- Changes its value at the clock edges

**Positive-edge triggered D Flip-Flop  
Truth table**


Clk	D	Q(t+1)
↑	0	0
↑	1	1
0	-	Q(t)
1	-	Q(t)

**Negative-edge triggered D Flip-Flop  
Truth table**


Clk	D	Q(t+1)
↓	0	0
↓	1	1
0	-	Q(t)
1	-	Q(t)
 
# Edge-Trigger in Always Block

- **Positive-edge trigger:** use **posedge** in your always block




 - **Negative-edge trigger:** use **negedge** in your always block


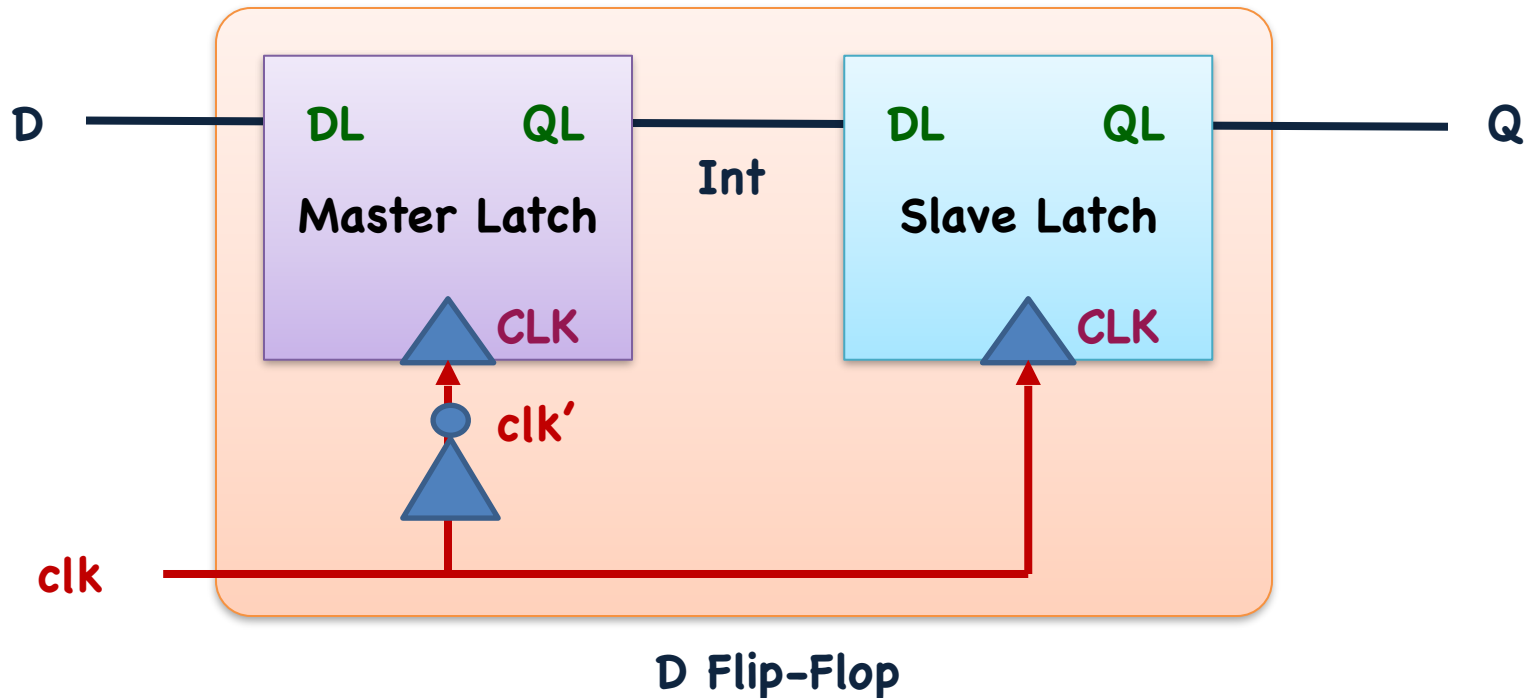
# Latches in a D Flip-Flop


- A positive-edge triggered D Flip-Flop consists of two latches
  - The master latch is triggered by  $\text{clk}'$
  - The slave latch is triggered by  $\text{clk}$
- Two level triggered latches form an edge-triggered Flip-Flop




 
# Flip-Flop Timing Diagram

- A timing diagram from the master latch to slave latch



# Agenda


- Combinational circuits
  - **Sequential circuits**
  - Debounce circuit and one-pulse circuit
  - 7-segment display
- Latch and flip-flop
  - **Always block usage**
  - Reset

## Today's class will help you:

1. Understand the difference between latch and flip-flop
2. Understand the timing diagram of latch and flip-flop
3. Understand synchronous reset
4. Understand the usage of push buttons, debounce circuit, and one-pulse circuit
5. Understand how to display four different digits on a 7-segment display
 
# Register Transfer Level

- Describes the behavior of combinational circuits between registers



# Always Block

- Two types of always block


## Combinational circuit

```
reg A, B, C;  
  
always @ (A or B)  
begin  
    //Blocking Assignment  
    B = A;  
    C = B;  
end
```


 
## Sequential circuit

```
reg A, B, C;  
  
always @ (posedge clk)  
begin  
    //Non-blocking assignment  
    B <= A;  
    C <= B;  
end
```



# Blocking and Non-blocking

## Execute in Order


```
always @ (A or B or C)  
begin
```

```
//Blocking Assignment
```

```
C = A & B;
```

```
D = !C;
```

```
end
```

 

## Execute in Parallel


```
always @ (posedge clk)  
begin
```

```
//Non-blocking assignment
```

```
C <= A & B;
```

```
D <= !C;
```

```
end
```

 

- **NEVER** use blocking and non-blocking assignment in the **SAME** always block



# Agenda

- Combinational circuits
  - **Sequential circuits**
  - Debounce circuit and one-pulse circuit
  - 7-segment display
- Latch and flip-flop
  - Always block usage
  - **Reset**

## Today's class will help you:

1. Understand the difference between latch and flip-flop
2. Understand the timing diagram of latch and flip-flop
3. Understand synchronous reset
4. Understand the usage of push buttons, debounce circuit, and one-pulse circuit
5. Understand how to display four different digits on a 7-segment display


# Initialize Flip-Flops

- For combinational circuits, we initialize the inputs of modules by initial blocks in the testbench
- For sequential circuits, a **reset signal** is necessary
  - Initialize the reset signal (i.e. your module) first in your testbench
- Two reset methods
  - Synchronous reset
  - Asynchronous reset (Next week)


# Synchronous Reset

- Reset the value stored in a D Flip-Flop to 0
- Triggered by clock edges
- Assume that **Q = 1'b0** when Reset is set to 1'b0

Scheme 1

 

Scheme 2

 


# Synchronous Reset in Always Block

- **Prioritize** your reset signal over the rest of the inputs
- In your testbench, **initialize your reset signal first**
- You **shall not** use any initial block in your design modules


```
module My_Test_Flip_Flop (Out, In, clk, Reset);  
  input    In, clk, Reset;  
  output   Out;  
  reg      Out;  
  
  always @ (posedge clk) ← Behavior  
  begin  
    if (Reset == 1'b0)      Out <= 1'b0;  
    else                    Out <= In;  
  end  
endmodule
```

**Declaration of Synchronous**

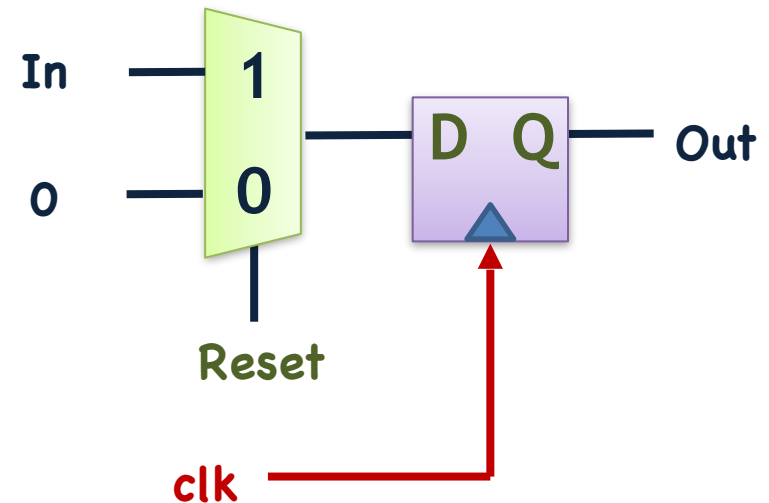
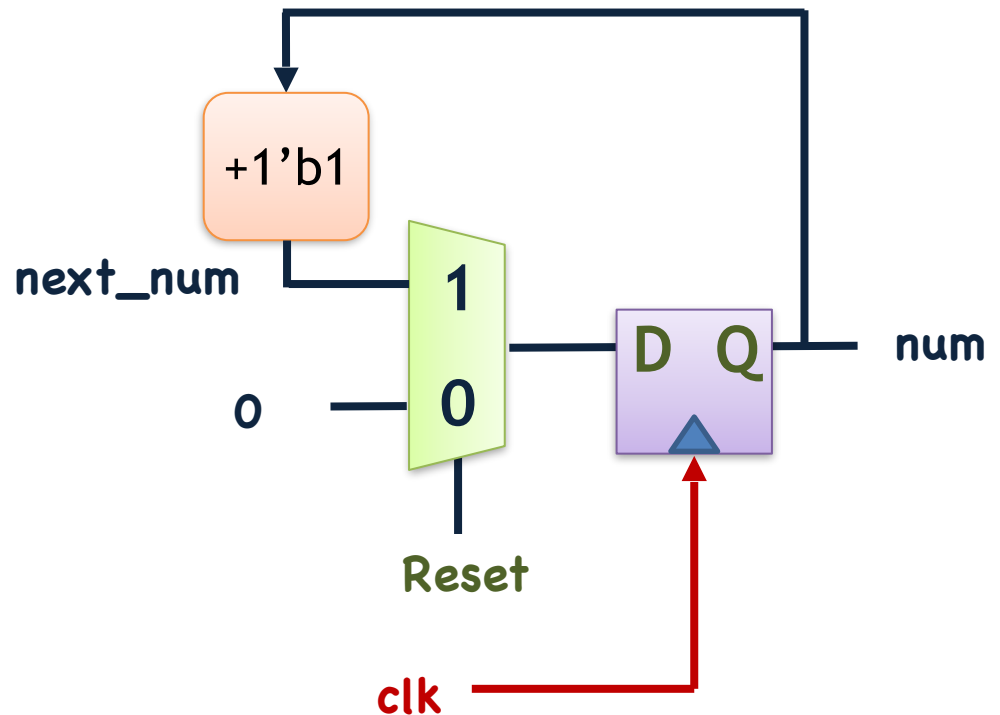
# Example: 3-Bit Counter

```
module Counter_3Bit(clk, Reset, num);  
input    clk, Reset;  
output   [2:0] num;  
reg      [2:0] num;  
wire     [2:0] next_num;  
  
always @(posedge clk) begin  
    if (!Reset)  
        num <= 1'b0;  
    else  
        num <= next_num;  
    end  
  
assign    next_num = num + 1'b1;  
  
endmodule
```





# Agenda


- Combinational circuits
- Sequential circuits
- **Debounce circuit and one-pulse circuit**
- 7-segment display

## Today's class will help you:

1. Understand the difference between latch and flip-flop
2. Understand the timing diagram of latch and flip-flop
3. Understand synchronous reset
4. Understand the usage of push buttons, debounce circuit, and one-pulse circuit
5. Understand how to display four different digits on a 7-segment display

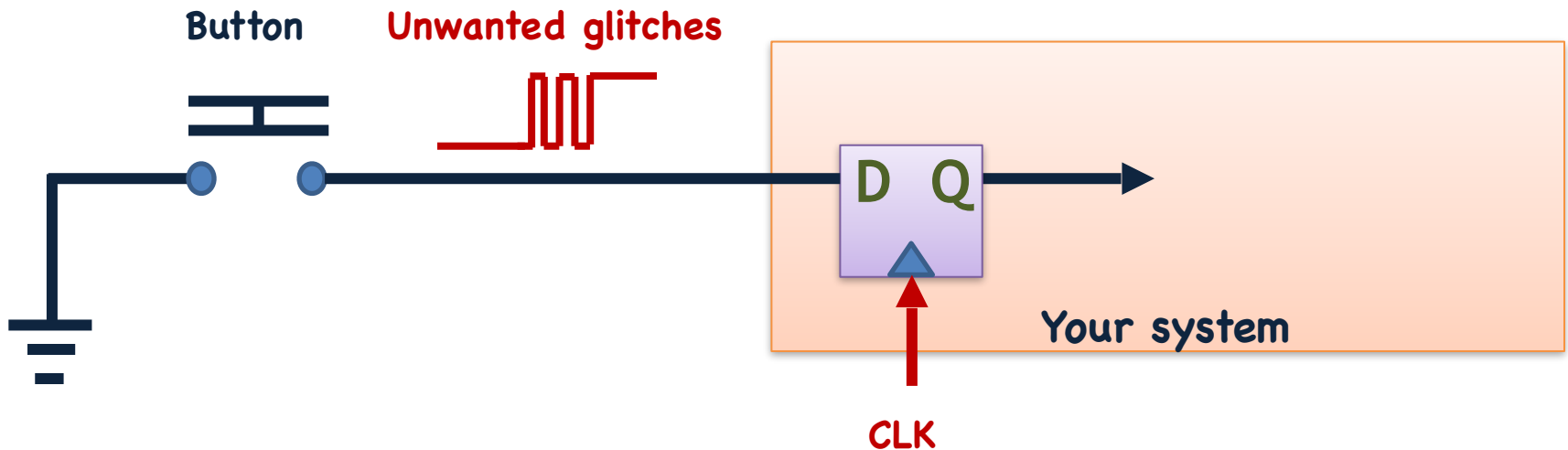
# Push Buttons

- Several push buttons are available as inputs on FPGA
- Map push buttons to your inputs using .xdc file
- Need to handle **meta-stability (glitches)** problem


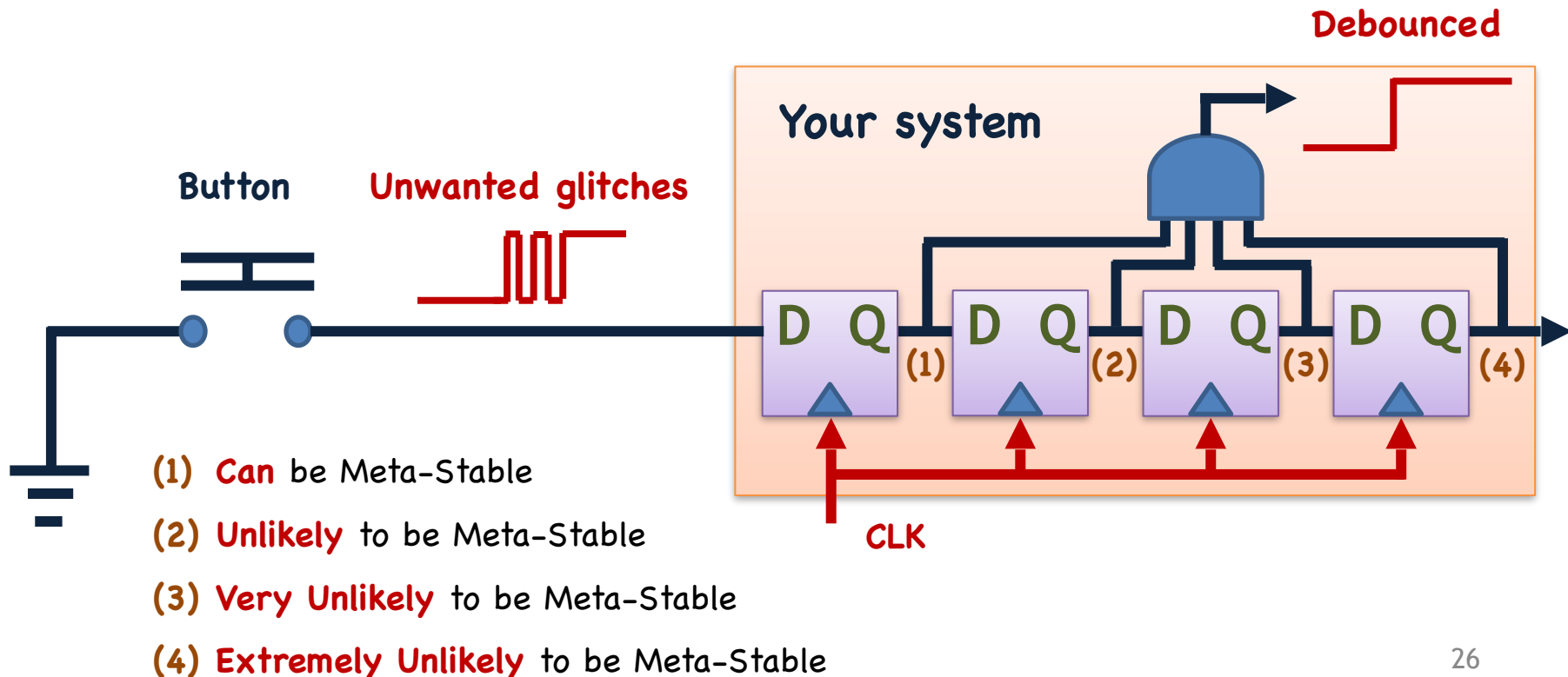
# Handling Meta-Stability

- Debounce circuit
- Shift registers to allow time for signals to stabilize
- Detect if DFF chains are all ones or zeros



# Verilog Code for Debounce Circuit

```
module debounce (pb_debounced, pb, clk);

    output    pb_debounced;    // signal of a pushbutton after being debounced
    input     pb;               // signal from a pushbutton
    input     clk;

    reg [3:0] DFF;              // use shift_reg to filter pushbutton bounce


    always @(posedge clk)
    begin
        DFF[3:1] <= DFF[2:0];
        DFF[0]   <= pb;
    end

    assign pb_debounced = ((DFF == 4'b1111) ? 1'b1 : 1'b0);

endmodule
```


 
# One Pulse Circuit

- The one pulse circuit generates a one-clock-cycle pulse when the push button is pressed
  - A push button is usually pressed for many clock cycles
- The circuit is used when we want to trigger only once





# One Pulse Circuit (Cont'd)

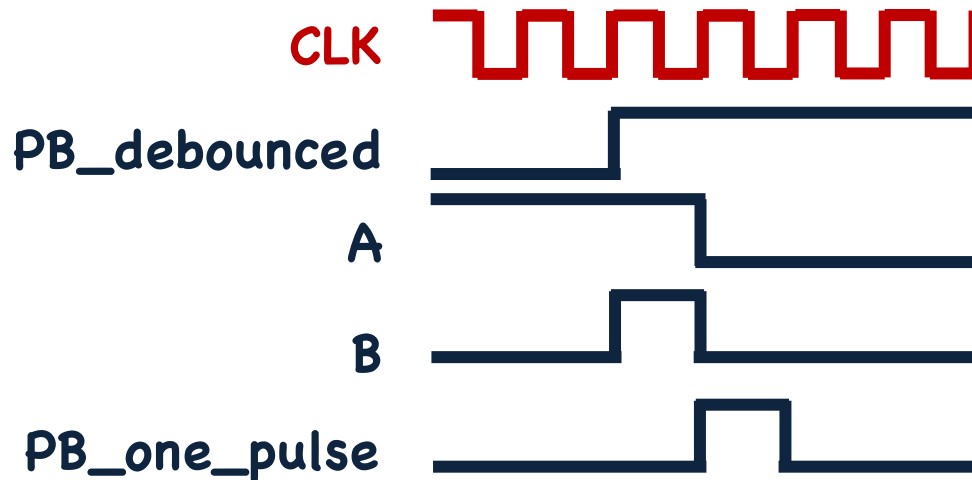 

# Verilog Code

**// One-pulse circuit**

**module** onepulse (PB\_debounced, **CLK**, PB\_one\_pulse);

**input** PB\_debounced;

**input** **CLK**;

**output** PB\_one\_pulse;

**reg** PB\_one\_pulse;

**reg** PB\_debounced\_delay;

**always** @(posedge **CLK**) **begin**

PB\_one\_pulse <= PB\_debounced & (! PB\_debounced\_delay);

PB\_debounced\_delay <= PB\_debounced;

**end**

**endmodule**

# Agenda

- Combinational circuits
- Sequential circuits
- Debounce circuit and one-pulse circuit
- **7-segment display**


## Today's class will help you:

1. Understand the difference between latch and flip-flop
2. Understand the timing diagram of latch and flip-flop
3. Understand synchronous reset
4. Understand the usage of push buttons, debounce circuit, and one-pulse circuit
5. Understand how to display four different digits on a 7-segment display

# 7-Segment Display Control (1/2)

- Four enable signals for the four display units
  - **AN[3:0]** correspond to **the four digits**
  - **AN** is used to **ENABLE** one of **the four digits**
  - Set one bit of AN[3:0] to **LOW** to illuminate one digit


AN Bit	FPGA Pin
3	W4
2	V4
1	U4
0	U2

 

Digit	AN[3:0]
3	0111
2	1011
1	1101
0	1110
 
# 7-Segment Display Control (2/2)

- Eight signals for the segments and dot
  - **seg[0:6]** in the XDC file correspond to **segments A~G** shown below
  - **dp** in the XDC file corresponding to **DP (dot)**
  - To illuminate a segment, set its value to **LOW**




Symbol	FPGA Pin
CA	W7
CB	W6
CC	U8
CD	V8
CE	U5
CF	V5
CG	U7
DP	V7


 
# Display Four Digits Concurrently

- Time multiplexing
- Use a **mux** and **clock divider**
  - **Mux** to select the digit to display (i.e. set which **AN** bit to low)
  - **Clock divider** to display at the right refresh frequency (**1ms to 16ms**)
- The clock provided by Basys 3 is **100MHz**
  - That is, **10ns** per clock cycle
  - Generate a clock with a frequency of  **$1/2^{17}$  clk**



\*Pictures cited from [www.xilinx.com](http://www.xilinx.com) for education purpose only



# Thank you for your attention!



\*Taken at Yosemite Valley Village at Yosemite, California, USA.  
This picture is taken by Chun-Yi Lee himself, who is also a fan of photography