



Welcome to The Logic Design Lab!

Fall 2021

Moore and Mealy Conversion

Prof. Chun-Yi Lee

Department of Computer Science
National Tsing Hua University

Agenda

- **Announcement**
- **Moore and Mealy conversion**
 - Moore to Mealy conversion
 - Mealy to Moore conversion
- **Common Questions**
- **Datapath Components**

Today's class will help you:

1. Understand that Moore and Mealy machines may be interchangeable
2. Understand how to convert a Moore machine to a Mealy machine
3. Understand how to convert a Mealy machine to a Moore machine

Announcements

- Lab 4
 - Lab 4 advanced questions due on **11/11/2021 (Thu)**
 - Lab 4 demonstration on **11/18/2021 (Thu) (FPGA)**
 - **Please read the lab description and specification carefully**
 - **Compile your codes again before merging yours with your teammates**
 - **Please follow the template I/Os and submit your `.v` files**
- Final project
 - You can begin working on your final projects from now
 - Please avoid copying the works from past years

Final Project

- Use your FPGA to implement creative and interesting works
- Final project proposal due on **12/13/2021 (Mon)**
- Final project report due on **1/14/2022 (Fri)**
- Final exam
 - **12/9/2021 (Thu)**
 - 2 hours

Final Project Presentation

- Final project demonstration on **1/13/2022 (Thu)** and **1/14/2022 (Fri)**
 - Around 10 minutes per team
- **No restriction on your presentation style**
 - Be creative!
 - What is special and new in your project
 - Key features
- Order of presentation
 - We will randomly decide the order
 - Let us know if you have constraints

Final Project Report

- Final project report
 - Due on **1/14/2022, 23:59pm (Fri)**
 - Block diagrams and state transition diagrams
 - **Detailed explanation**
- Report contents
 - Introduction
 - Motivation
 - System specification
 - Experimental results
 - Conclusion
 - ...And any other sections that you would like to include

Final Project Award

- **Category:** Difficulty and completeness
 - Graded by me and the TAs
 - Difficulty (**35%**)
 - Completeness (**30%**)
 - Source code coding style (**15%**) (Correctness, usage, comments, etc.)
 - Report (**20%**)
 - First place: **NTD \$6,000**
 - Second place: **NTD \$3,000**
 - Third place: **NTD \$1,500**
- **Category:** Best creativity
 - Voted by everyone in the class
 - **NTD \$1,000**
- **Category:** Deep learning models in FPGA
 - Extra **bonus points** and **cash rewards**. To be announced

Final Exam

- Dates and time
 - 12/9/2021 (Thu)
 - 3:30pm ~ 5:30pm (2 hours)
- Course contents
 - Verilog design questions
 - Logic design concepts
 - Lecture & lab contents

Agenda

- Announcement
- **Moore and Mealy conversion**
 - **Moore to Mealy conversion**
 - **Mealy to Moore conversion**
- Common Questions
- Datapath Components


Today's class will help you:

1. Understand that Moore and Mealy machines may be interchangeable
2. Understand how to convert a Moore machine to a Mealy machine
3. Understand how to convert a Mealy machine to a Moore machine


Moore vs. Mealy Machines

- Moore machine: **outputs** depend on **current states** only
- Mealy machine: **outputs** depend on **current states** and **inputs**

Moore machine

 



Mealy machine

 

Mealy Machine Input Changes


- Outputs depend on inputs and current state
- Inputs change may cause outputs change immediately
- State changes only at clock edges

Mealy machine

  


Moore to Mealy Conversion

Moore machine

 


Mealy machine

 


Moore to Mealy Conversion

Moore machine

 


Mealy machine

 

Moore to Mealy Conversion


Moore machine

 

	a	b	output
S0	S1	S0	0
S1	S1	S2	0
S2	S1	S0	1

Next state

Mealy machine

 

	a	b
S0	S1, 0	S0, 0
S1	S1, 0	S2, 1
S2	S1, 0	S0, 0

Next state, **Output**

Agenda


- Announcement
- **Moore and Mealy conversion**
 - Moore to Mealy conversion
 - **Mealy to Moore conversion**
- Common Questions
- Datapath Components

Today's class will help you:

1. Understand that Moore and Mealy machines may be interchangeable
2. Understand how to convert a Moore machine to a Mealy machine
3. Understand how to convert a Mealy machine to a Moore machine


Mealy to Moore Conversion

Mealy machine

 


Moore machine

S1 & S2 separates to two states

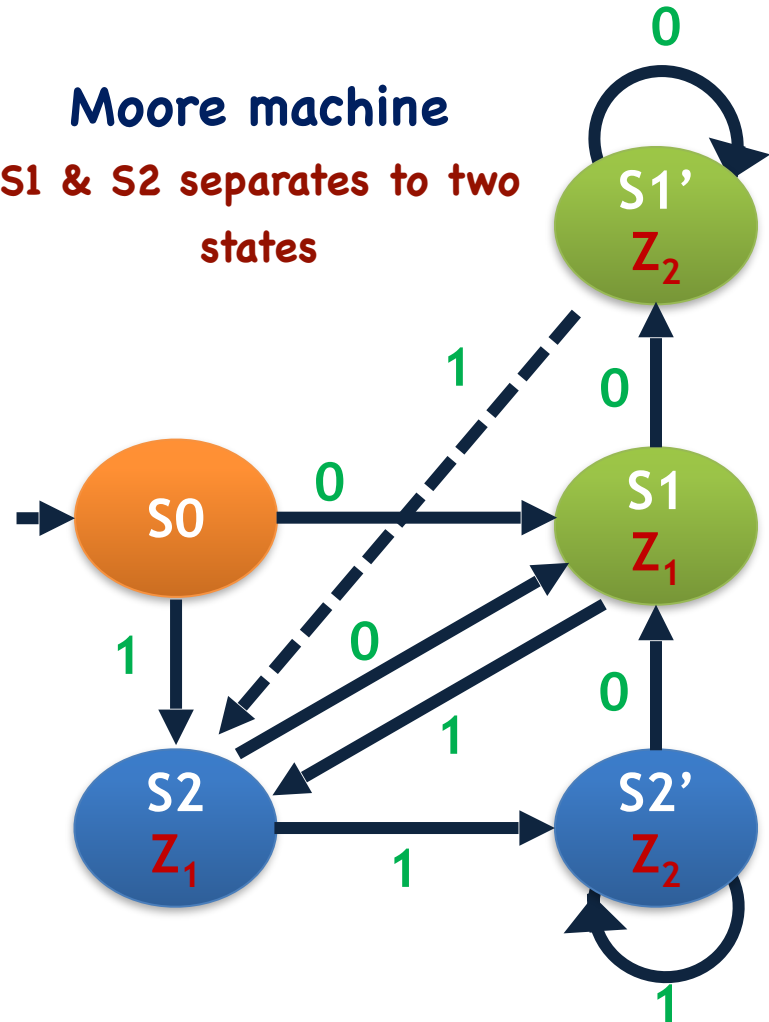


Mealy to Moore Conversion

Mealy machine

 

Moore machine

S1 separates to two states

 

State Changes in Conversion

- Moore machine to Mealy machine
 - Number of states does not change
- Mealy machine to Moore machine
 - **May need to split the states**
 - Number of states increased
 - A Mealy machine with **N** states and **M** outputs may lead a Moore machine with a maximum of (**N** x **M**) states
 - In the previous example, **N** = 2 and **M** = 2

Agenda

- Announcement
- Moore and Mealy conversion
 - Moore to Mealy conversion
 - Mealy to Moore conversion
- **Common Questions**
- Datapath Components

Today's class will help you:

1. Understand that Moore and Mealy machines may be interchangeable
2. Understand how to convert a Moore machine to a Mealy machine
3. Understand how to convert a Mealy machine to a Moore machine

Why Can't I Configure FPGA...?

- Simulation passed, configuration failed
- Multiple assignments to **THE SAME** variable in **DIFFERENT** always blocks
- A variable can only be assigned in one single always block

```
always@(Sel or A or B or C or D)
begin
  Counter = A + D;


  if (Sel[0] == 1'b1) D = B;
  else
    D = C;
end
```

```
always@(posedge CLK) begin
  if (!RESET)
    Counter <= 4'd0;
  else
    begin
      Counter <= Counter + 1'b1;
    end
end
```

Multiple assignments

Low Frequency Signals

 - **Clock division in practical implementations**
 - All D-Flip Flops are triggered by the system clock signal
 - If clock division is required, use counter to create another signal called DIV_Sig
 - When `DIV_Sig == 1'b1`, perform your operations



```
always @ (posedge CLK) begin
    if (DIV_Sig == 1'b1)
        // Your operations here
    else
        // Your operations here
end
```


Delay Control Operator

- **#** followed by units of time
- Specify the delay in terms of units specified by `timescale
- **NOT synthesizable**, only used in testbench
- In real circuits, delay is realized by buffers (two inverters)

```
...  
always  
begin  
    #0    clock = 0;  
    #50   clock = 1;  
    #50;  
end  
...
```

```
...  
always  
begin  
    #clock_period/2;  
    clock = ~clock;  
end  
...
```

parameter
clock_period



Agenda

- Announcement
- Moore and Mealy conversion
 - Moore to Mealy conversion
 - Mealy to Moore conversion
- Common Questions
- Datapath Components

Today's class will help you:


1. Understand that Moore and Mealy machines may be interchangeable
2. Understand how to convert a Moore machine to a Mealy machine
3. Understand how to convert a Mealy machine to a Moore machine

Datapath Components

- Design a system that contains control, execution, and storage components
 - **You have already learned all of these components in this semester**
- Data are stored in **storage components**
 - Memory
 - Cache
 - Registers
- Data are processed in **execution components**
 - Arithmetic components (adders, multipliers, subtractors, etc.)
 - Logical operation components (AND, OR, NOT, etc.)
 - Shifters and comparators
- Data flow is determined by **control components**


Simple Datapath Structure

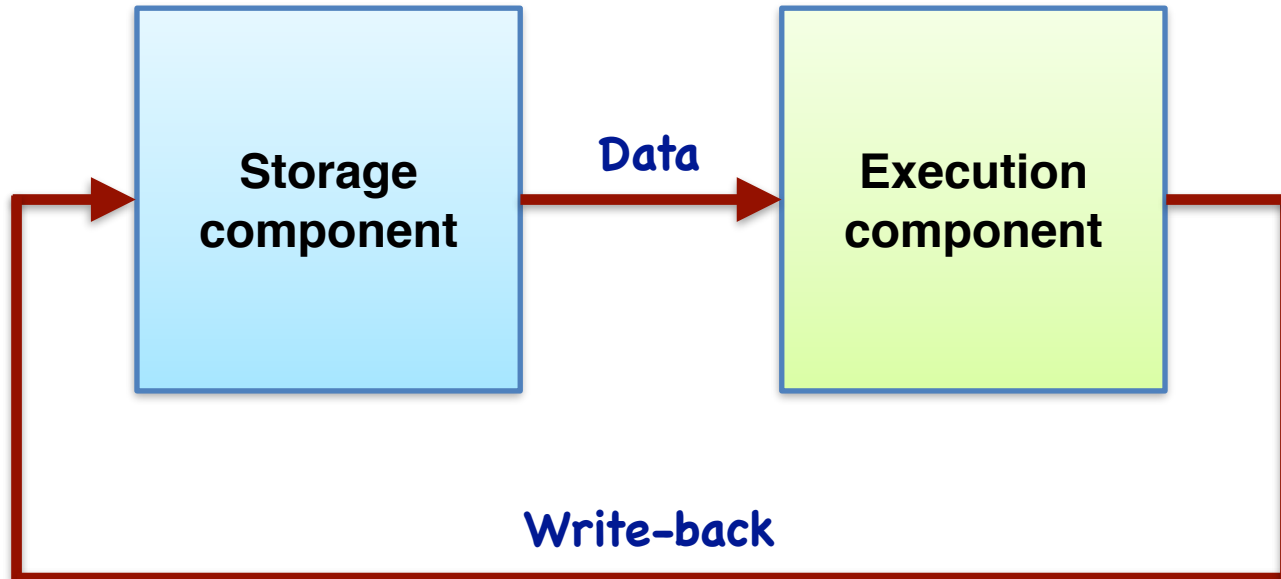- Storage components provides data to be processed
- Execution component process the data
- The result is stored back to the storage component




Instructions Comes In

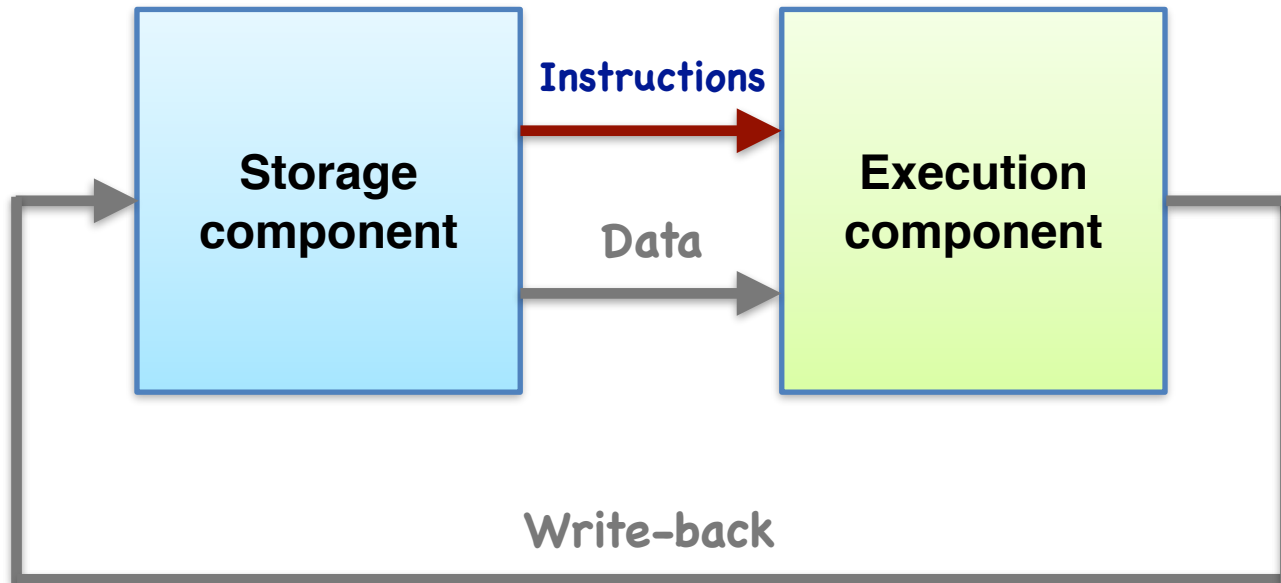- Instructions tells the execution component what operations to execute
- Depending on the instructions, the execution component selects the appropriate sub-units to run




Decoder Comes In

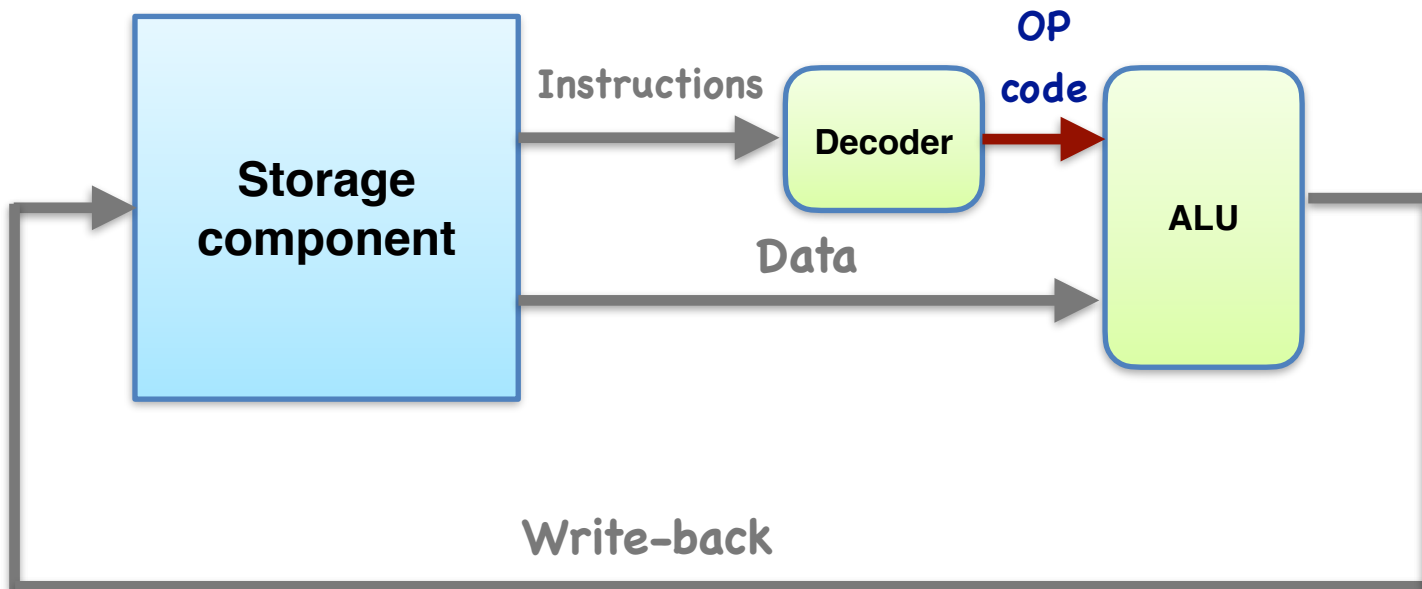- ALU stands for **A**rithmetic **L**ogic **U**nit
- Instructions are decoded by an decoder (Lab 1)
- The decoder generates an OP code for ALU (Lab 2)
- The ALU contains adders, multipliers, shifters, etc for execution (Lab 1 & 2)




Separation of Storage Component

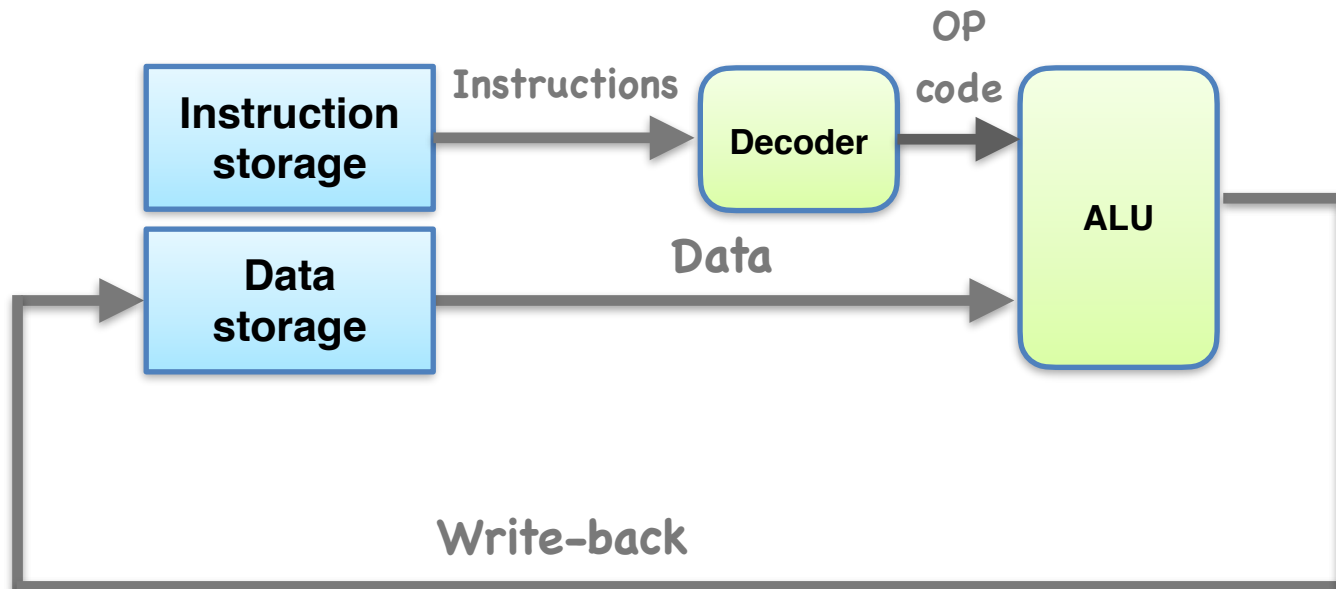- The storage component can be splitted into instruction storage and data storage
- The instruction storage stores the instructions to be operated
- The data storage stores the data to be processed




Program Counter

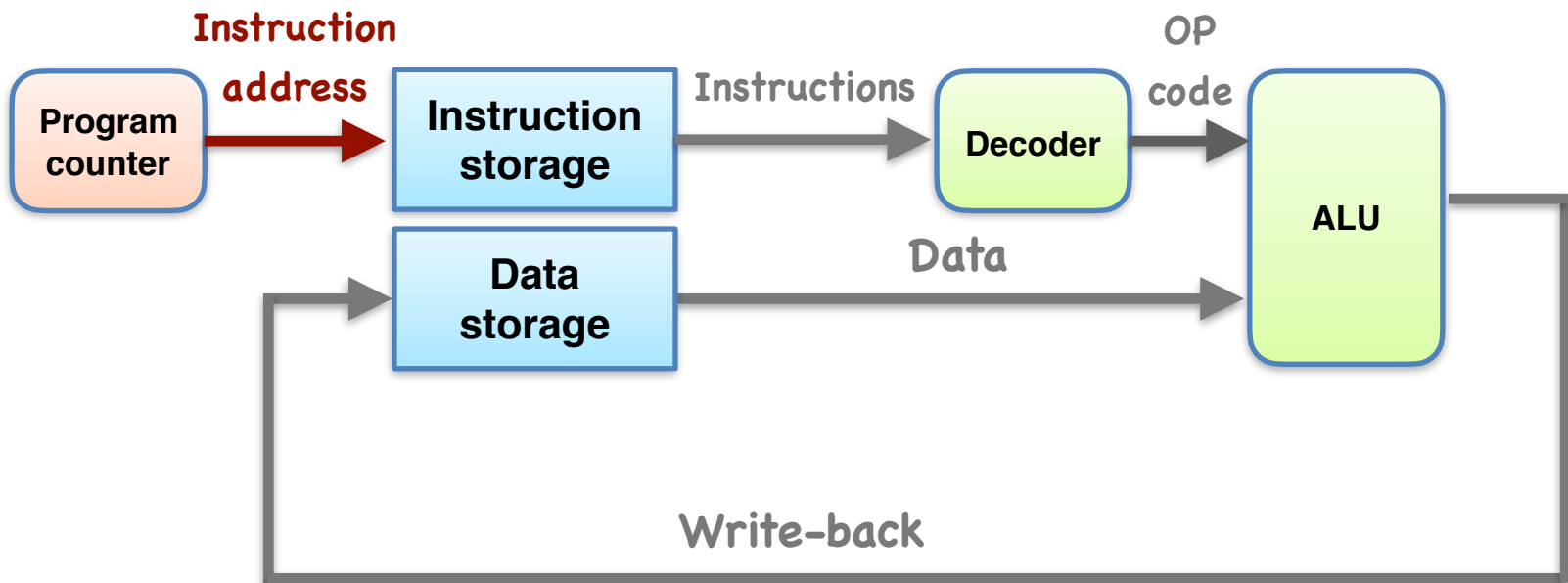- Program counter (PC) provides the address of the instruction to be executed in the instruction storage
- Program counter updates the address to the next instruction every cycle
 - $PC \leq PC + 4$ (4 bytes per instruction)
- The instructions stored in the instruction storage are called **a program**




Registers for Local Storage

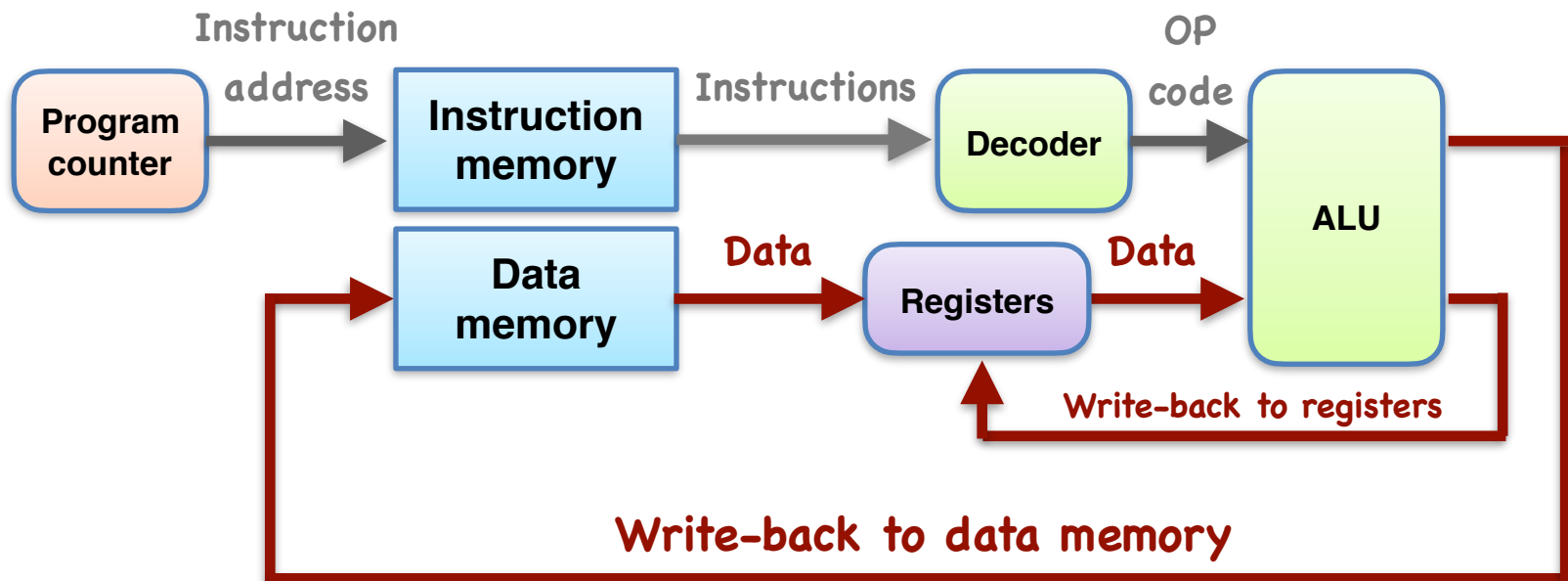- Data storage is separated into registers and data memory
- Registers are small amount of storage elements constructed from DFFs
- Data can be loaded from the data memory to the registers
- Data can also be stored back to the registers from the ALU results




Selection of Registers

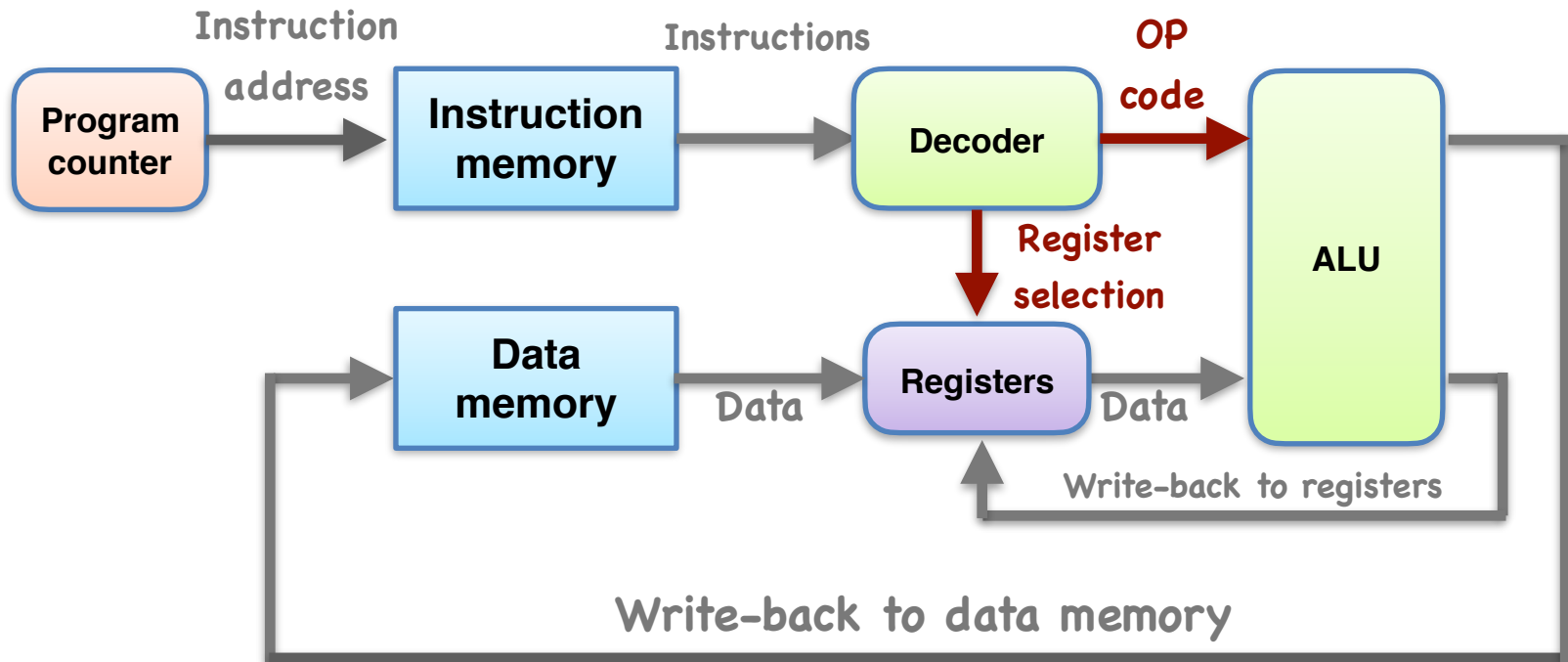- The decoder generates two items: **OP code** and **register selection**
- The decoder selects the registers whose contents are to be fed into ALU



Five Stage Pipeline

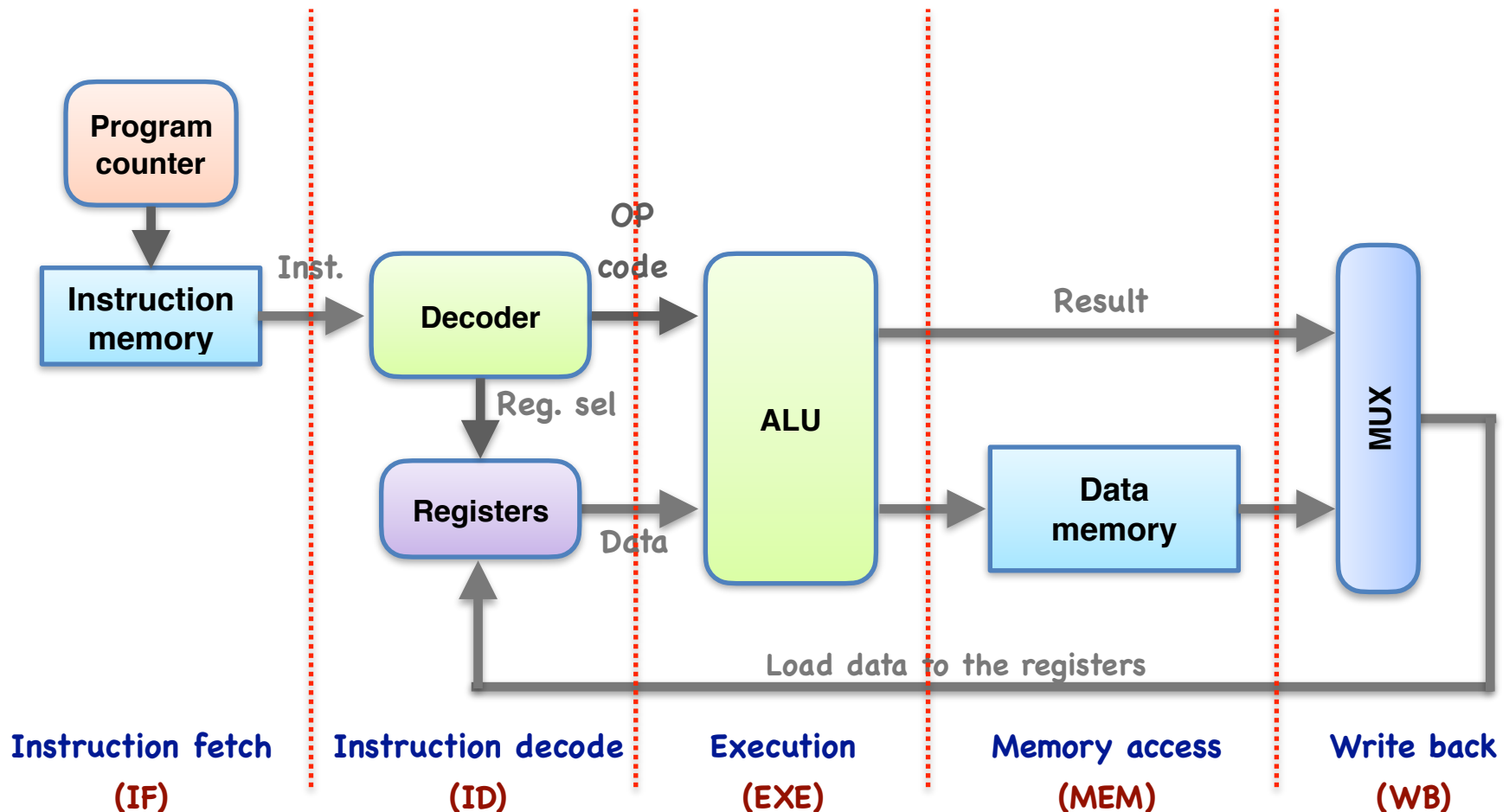- The datapath can be re-organized and separated into five stages
- This five stage pipeline structure is the basis of computer architecture





Thank you for your attention!

*Pier view taken at Hollywood, Los Angeles, California, USA.

This picture is taken by Chun-Yi Lee himself, who is also a fan of photography