



Welcome to The Logic Design Lab!

Fall 2021
Sequential Circuit II

Prof. Chun-Yi Lee

Department of Computer Science
National Tsing Hua University

Agenda

- **Announcement**
- **Clarification**
- **Sequential circuits**
- **Finite state machine concept**

Today's class will help you:

1. Understand the difference between synchronous reset and asynchronous reset
2. Understand concept of the global clock signal
3. Understand the concept of finite state machine

Announcements

- Lab 3
 - Basic questions demonstration on **10/21/2021 (Thu)**
 - Advanced questions and FPGA demonstration due on **10/28/2021 (Thu)**
- Midterm Exam
 - Computer-based exam on **11/4/2021 (Thu)**

Agenda

- Announcement
- **Clarification**
- Sequential circuits
- Finite state machine concept

Today's class will help you:

1. Understand the difference between synchronous reset and asynchronous reset
2. Understand concept of the global clock signal
3. Understand the concept of finite state machine

Variable Assignment

- Only assign values to a variable in a **single always block**



```

module Counter (clk, Reset, Out);
input      clk, Reset;
output    Out;
reg       [3:0] counter;

always @(posedge clk) begin
    if (!Reset)
        counter <= 4'b0000;
    else
        counter <= counter + 1'b1;
    end

    assign out = counter [3];

endmodule

```



```

module Counter (clk, Reset, Out);
input      clk, Reset;
output    Out;
reg       [3:0] counter;

always @(posedge clk) begin
    if (!Reset)
        counter <= 4'b0000;
    else
        counter <= counter + 1'b1;
    end

    always @ (*) begin
        if (counter == 4'b1010)
            counter = 4'b0000;
    end

    assign out = counter [3];

endmodule

```


Agenda

- Announcement
- Clarification
- Sequential circuits
 - Reset
 - Clock
- Finite state machine concept

Today's class will help you:

1. Understand the difference between synchronous reset and asynchronous reset
2. Understand concept of the global clock signal
3. Understand the concept of finite state machine

Why Do We Need a Reset?


- Initialize your flip-flops
- If not properly reset, your flip-flops may get unknown values (e.g., **XXXX** in your counters)




Synchronous Reset

- Reset the value stored in a D Flip-Flop to 0
- Triggered by clock edges
- Assume that **Q = 1'b0** when Reset is set to 1'b0

Scheme 1

 

Scheme 2

 


Synchronous Reset in Always Block

- **Prioritize** your reset signal over the rest of the inputs
- In your testbench, **initialize your reset signal first**
- You **shall not** use any initial block in your design modules


```
module My_Test_Flip_Flop (Out, In, clk, Reset);  
  input    In, clk, Reset;  
  output   Out;  
  reg      Out;  
  
  always @ (posedge clk) ← Behavior  
  begin  
    if (Reset == 1'b0)      Out <= 1'b0;  
    else                    Out <= In;  
  end  
endmodule
```

Declaration of
Synchronous

 


Synchronous Reset in Waveform

 - Reset the flip-flops at **clock edges**



Asynchronous Reset in Waveform

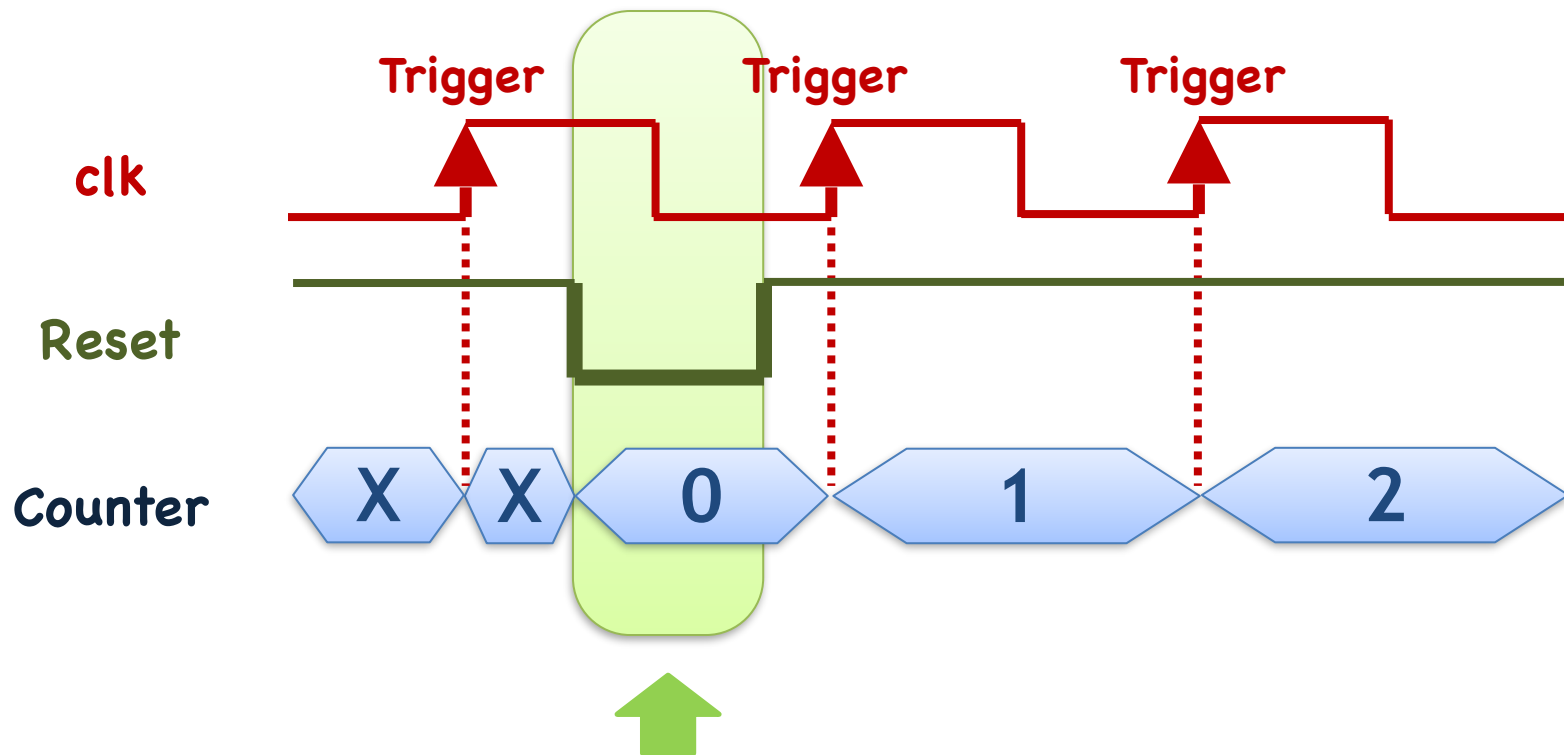- Reset the flip-flops **ANY TIME**
- Concept similar to **Latches**




Reset is done regardless of the **clk** signal

Asynchronous Reset in Always Block

- Add "**negedge Reset**" or "**posedge Reset**" in always statements
- Reset the flip-flops regardless of **clk**
- **Reset** signal gets the **highest priority**

 
```
module My_Test_Flip_Flop (Out, In, clk, Reset);  
  input  In, clk, Reset;      Declaration of  
  output Out;                  Asynchronous  
  reg    Out;                  Behavior  
                                ↓  
  always @ (posedge clk or negedge Reset)  
  begin  
    if (Reset == 1'b0)          Out <= 1'b0;  
    else                        Out <= In;  
  end  
endmodule
```




Out is reset to 0 when Reset goes down to zero

Asynchronous Reset in Latches

Latch in Lab 1

 


Latch with
Asynchronous
Reset

 


Asynchronous Reset in DFFs


DFF in Lab 1
(Synchronous)

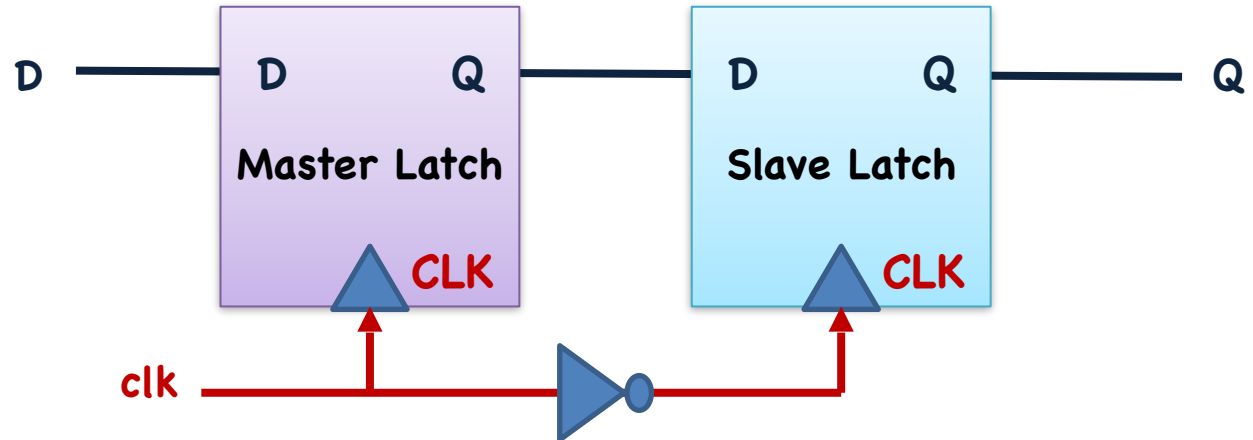


DFF with
Asynchronous
Reset

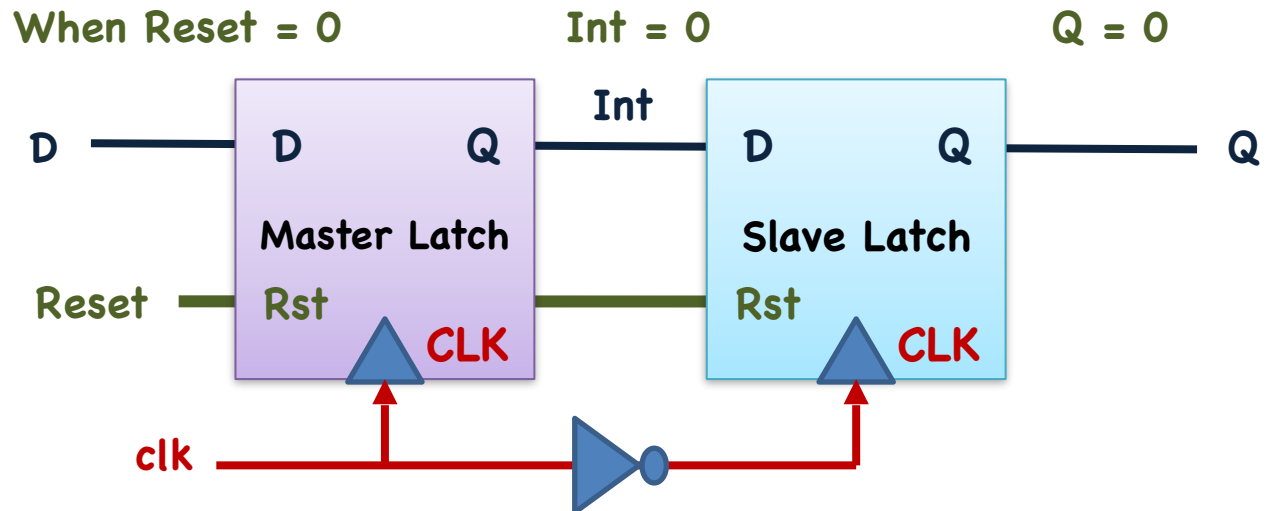

Synchronous vs. Asynchronous Reset

 

Synchronous Reset

 


Asynchronous Reset

	Synchronous Reset	Asynchronous Reset
Clock	Reset at clock edges	Regardless of clock
Always block	always @ (posedge clk)	always @ (posedge clk or negedge Reset)
Logic	Additional Mux or AND gate	Additional reset input port in DFF


Advantages of Asynchronous Reset

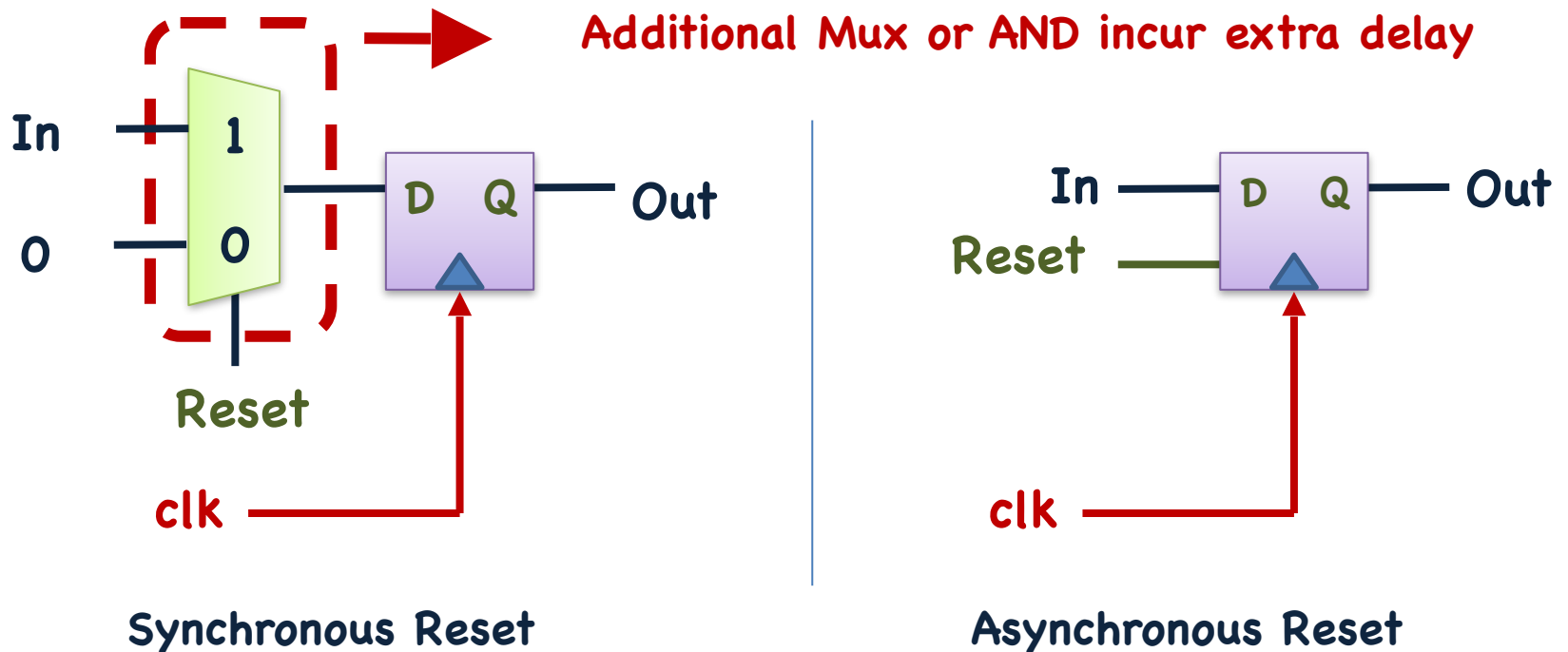- Fast
 - No additional Mux or AND
- Reset **ANYTIME**, no clock signal is required




Disadvantages of Asynchronous Reset

Ideal

 

In reality

 
Asynchronous Reset
is vulnerable to
glitches




Advantages of Synchronous Reset

- Synchronous Reset is not affected by glitches
- Unless glitches occur right at clock edges

Asynchronous Reset

 


Synchronous Reset

 


Disadvantages of Synchronous Reset

- Slower
- If Reset signal is too short, no DFFs are reset

Reset is long enough

 

Reset is too short

 

Summary of Pros and Cons

- Here we summarize the previous slides

Reset type	Advantages	Disadvantages
Synchronous	Not affected by glitches, Completely synchronous circuit	Slow, Reset cannot be too short
Asynchronous	Fast, Reset anytime	Vulnerable to glitches, Larger DFFs

Agenda

- Announcement
- Clarification
- **Sequential circuits**
 - Reset
 - **Clock**
- Finite state machine concept

Today's class will help you:

1. Understand the difference between synchronous reset and asynchronous reset
2. Understand concept of the global clock signal
3. Understand the concept of finite state machine

Why do We Need a Clock?

- In real world, we need clocks to tell us what time is it
- ...so that we can collaborate no matter where we are



Bob in Antarctica



Kevin in New York

How do they collaborate?


They need to know each other's time

Stuart in Paris




Clock Signal for Logic Blocks

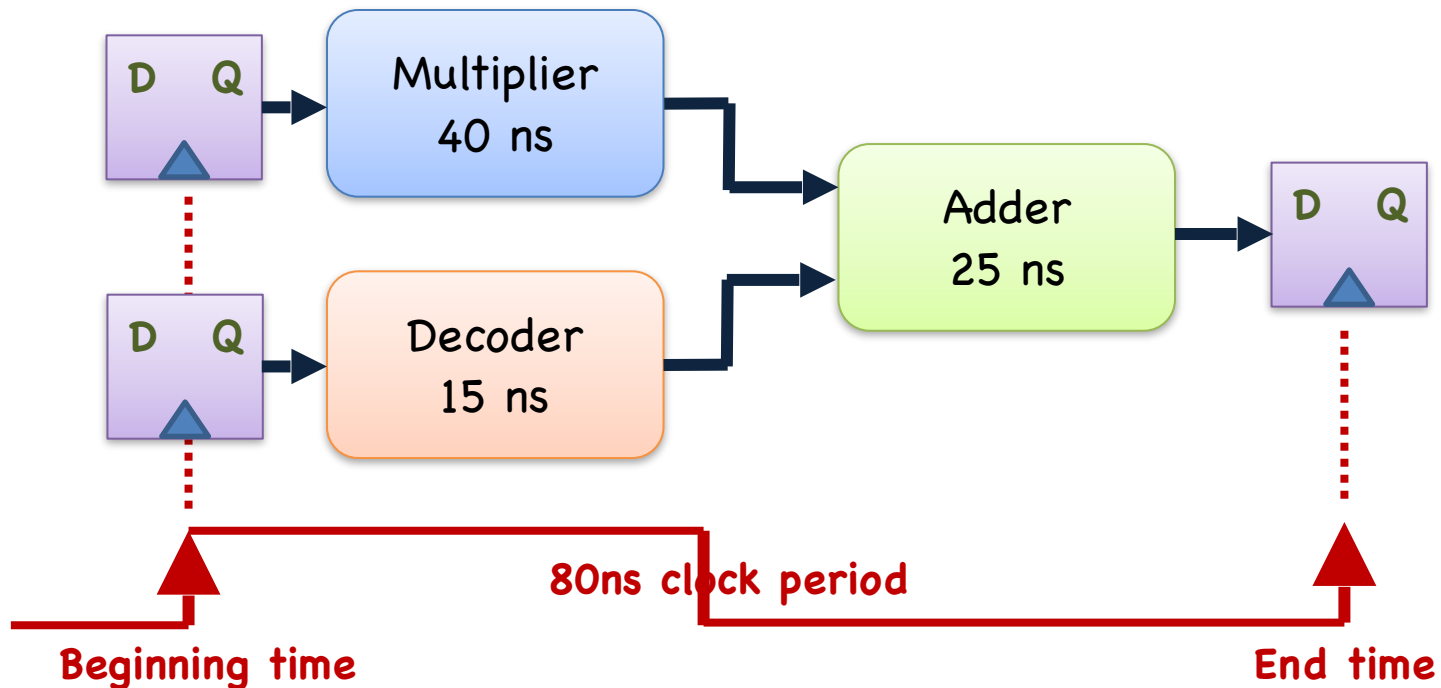- Clock signals and DFFs are used to synchronize the beginning and end time of a computation
- Ensure the progresses of all the blocks
 - Similar to the concept of our beginning date and deadline of homework




Clock Signal Distribution

 - Clock signals are distributed all over the chip
- Different ways of distribution are possible



Deal with Faster Clock Requirements

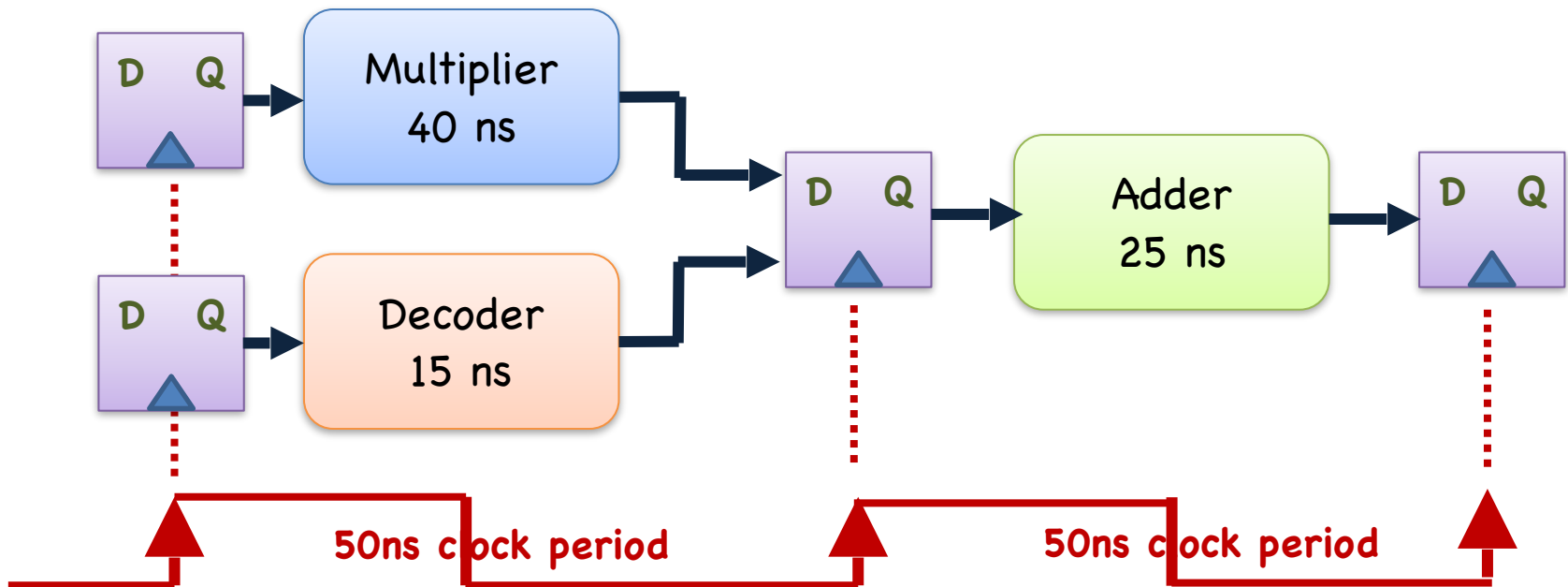- Divide your designs, and insert more pipeline stages
- Simply and redesign your logic
- Use faster devices



How Companies Decide Clock Freq?

- Basically, by **past experience** and **negotiation**




CEO:

We need 3GHz to compete
with our rivals




Higher management level:

 We need to get everything
done in 100 clock cycles



Your manager:

 We need to get our stuffs
done in 10 clock cycles



Your responsibility:

Mission impossible



Agenda

- Announcement
- Clarification of lab 3
- Sequential circuits
 - Reset
 - Clock
- **Finite state machine concept**

Today's class will help you:

1. Understand the difference between synchronous reset and asynchronous reset
2. Understand concept of the global clock signal
3. Understand the concept of finite state machine

What is Finite State Machine (FSM)?

- Everything in the world has states, so are you




FSM Can Change States

- States change when events happen
- <https://www.youtube.com/watch?v=WMIzCP5u2w8>



*Pictures cited from disney.com for education purpose only

State Transition Diagram

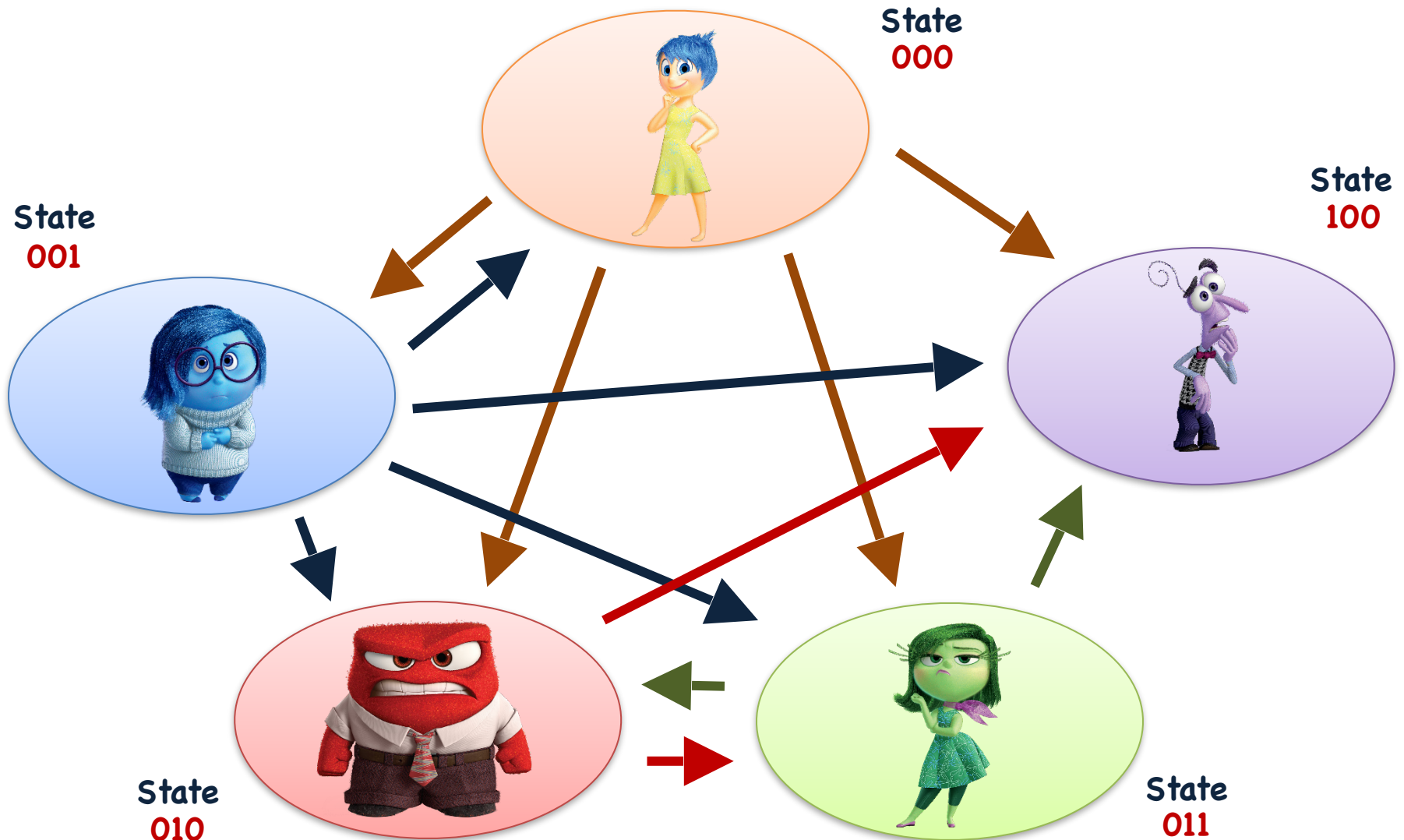

*Pictures cited from disney.com for education purpose only



Thank you for your attention!

*Taken at Lassen Peak at Shasta Caverns, California, USA.
This picture is taken by Chun-Yi Lee himself, who is also a fan of photography